



DEDAN KIMATHI UNIVERSITY OF TECHNOLOGY

University Examinations – 2019/2020

THIRD YEAR FIRST SEMESTER EXAMINATION FOR THE DEGREE OF BACHELOR OF
SCIENCE IN ELECTRICAL AND ELECTRONIC ENGINEERING

EEE3101: ANALOGUE ELECTRONICS I

DATE: AUGUST 2019

TIME: 2 Hours

INSTRUCTIONS

This paper consists of **FIVE** questions. Answer questions **ONE** and **ANY OTHER TWO**.

The following constants may be of importance

- Silicon $n_i = 1.4 \times 10^{16} \text{ m}^{-3}$
- $k = 1.38 \times 10^{-23}$
- $e = 1.6 \times 10^{-19}$

QUESTION ONE.

30 MARKS

- (a) Define the following terms as applied to semi-conductor sector.
- i). Doping [1 mark]
 - ii). Quiescent point [1 mark]
 - iii). Knee voltage [1 mark]
 - iv). Extrinsic semiconductor [1 mark]
- (b) Derive the relationship between β and α . [5 marks]
- (c) Outline the conditions that enables faithful amplification [3 marks]
- (d) Differentiate bipolar transistors (BJT) from field effect transistors (FET). [6 marks]
- (e) With the aid of well labeled diagram, describe how an n-p-n transistor can be used as a switch. [6 marks]
- (f) Determine the Q point of the silicon transistor circuit shown in Fig Q1. Also draw the D.C. load line, given $\beta_{dc} = 200$ [6 marks]

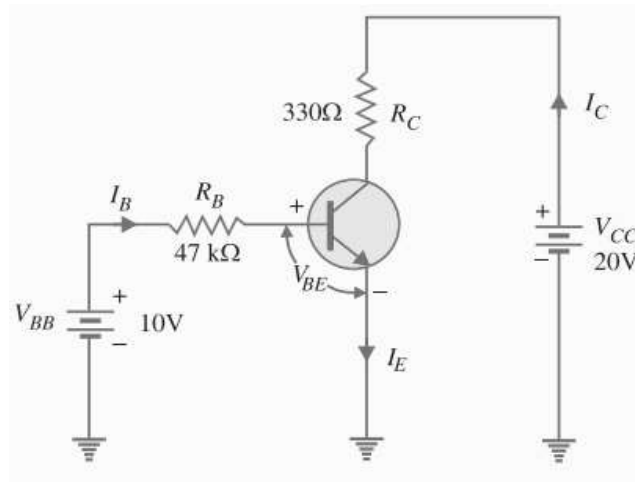


Fig. Q1

QUESTION TWO.

20 MARKS

(a) Define the following terms in relation to FETs.

- i. Source
- ii. Drain
- iii. Gate
- iv. Channel

[4 marks]

(b) In order for a transistor to operate in a circuit, it must be properly biased. State and explain the main reasons why transistors are biased.

[3 marks]

(c) Describe the principle of thermal runaway.

[3 marks]

(d) For the emitter bias silicon transistor circuit shown in Fig Q2, calculate I_E , I_C , V_C , V_{CE} for $\beta = 85$. Also determine how much the Q-point will change over a temperature range when β increase to 100 whilst V_{BE} decreases to 0.6V.

[10 marks]

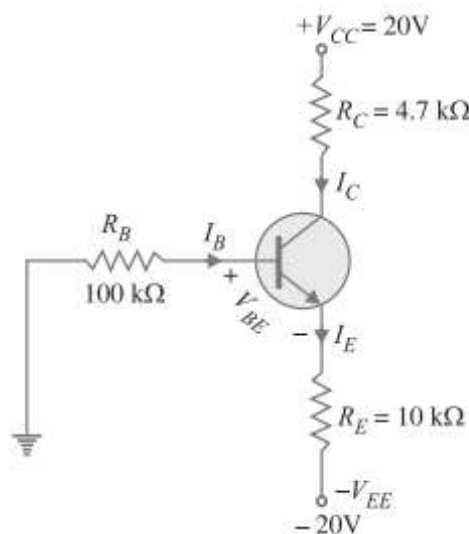
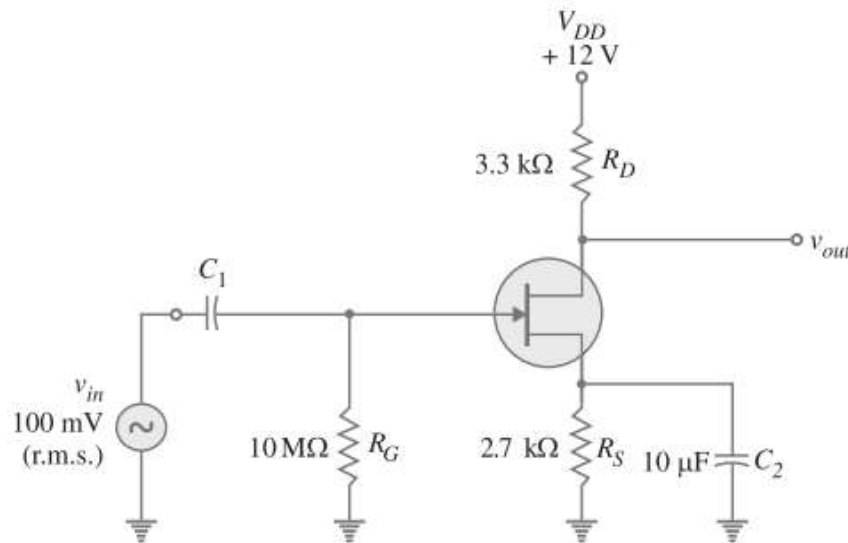


Fig. Q2

QUESTION THREE.**20 MARKS**

- (a) With aid of a circuit diagram, explain why a common emitter configuration for transistors is the most used. [4 marks]
- (b) A transistor has a base current of 50 mA and collector current of 3.65 mA.
- i). Calculate the parameter β_{dc} [3 marks]
- ii). Calculate the parameter I_E [3 marks]
- (c) Draw the schematic diagrams for a p -channel and an n -channel JFET. Label the terminals. [4 marks]
- (d) One application of transistors is acting as an amplifier. Using Fig. Q3, determine the r.m.s output voltage of the unloaded amplifier given that $I_{DSS} = 8$ mA, $V_{GS(off)} = -10$ V and $I_D = 1.9$ mA. [6 marks]

**Fig. Q3****QUESTION FOUR.****20 MARKS**

- (a) Outline four methods of bipolar transistor biasing. [4 marks]
- (b) With aid of diagram explain hole formation so as to establish hole current in semiconductor circuits. [6 marks]
- (c) Name three (3) discharge methods by which gases can conduct electricity [3 marks]
- (d) A silicon diode in an adapter rectifying circuit has a carrier density of 10^{21} in p material and 10^{22} m^{-3} in n material, the temperature of the charger changes from 27°C to 42°C , find the change in barrier potential of the diode. [7 marks]

QUESTION FIVE.**20 MARKS**

- a) Define the following giving an example in each case.
- i). Ohmic conductors
 - ii). Negative temperature coefficient **[4 marks]**
- b) With the aid of well labelled diagrams, explain how a silicon crystal can be doped to form extrinsic semiconductors. Give examples of appropriate doping elements for each case. **[8 marks]**
- c) In a self-bias n-channel JFET, the operating point is to be set at $I_D = 1.5 \text{ mA}$ and $V_{DS} = 10 \text{ V}$. Provided that the JFET parameters are $I_{DSS} = 5 \text{ mA}$ and $V_{GS(off)} = -2 \text{ V}$. Given that $V_{DD} = 20 \text{ V}$. Draw the circuit diagram and calculate the values of R_S and R_D . **[8 marks]**