

(10 members per group)

**EEE/ETI 3105    ASSIGNMENT 1    Due Date 17/06/2025    @3PM**

(a) A single-phase transformer with a ratio of 6600/400 V takes a no-load current of 0.7 A at 0.24 power factor lagging. If a current of 120 A at a power factor of 0.8 lagging is supplied by its secondary. Estimate the current drawn by the primary winding. **[5 Marks]**

(b) A 12 kVA, 220/440V, 50Hz single phase transformer gave the following test data:

**No Load:** 220V,                      2 A,                      165W (LV- side)

**S.C test:** 12V,                      15 A,                      60W- (HV side)

Draw the equivalent circuit as referred to LV side and insert the appropriate values. Find the secondary terminal voltage on full load and as a power factor of 0.8 lag. **[15 Marks]**

(c) A 400 kVA, distribution transformer has full load iron loss of 2.5kW and copper loss of 3.5kW. During a day, its load cycle for 24 hours is:

6 hours:    300kW at 0.8 p.f.

10 hours:    200kW at 0.7 p.f

4 hours:    100kW at 0.9 p.f

4 hours:    No load

Determine its all-day efficiency. **[15 marks]**

.....**THE END**.....